

3. LOGIC SIMULATION

Fernando Gonçalves ©




Projecto, Teste e Fiabilidade de Sistemas Electrónicos – 2019/2020


1

Introduction


Levels of simulation

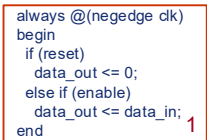


BEHAVIOR level

 


TRANSISTOR level

 

 FUNCTIONAL or REGISTER TRANSFER (RTL) level



PHYSICAL or GEOMETRICAL level

 

GATE level



Fernando Gonçalves

Projecto, Teste e Fiabilidade de Sistemas Electrónicos – 2019/2020

2


2

Objectives of the Logic Simulation

- **Project validation and verification** – detects project errors, initialization problems, errors caused by propagation delays, spikes, etc.
 - Logic verification (functional)
 - Timing analysis
- **Fault analysis**
 - Fault coverage
 - Fault diagnosis
- **Estimation of the circuit activity in order to evaluate the power consumption**
- **Code coverage evaluation**

3

Inputs/Outputs of a Simulator

 

4

Characteristics of a Logic Simulator

- Major problems
 - How to generate the stimuli?
 - How to know the correct responses?
 - How to evaluate the quality of the stimuli?
- Types of simulations
 - **Digital**: used at the behavioral, functional or gate levels
 - **Analog**: used at the transistor level (Spice-like simulators)
 - **Mixed**: used for mixed analog/digital circuits
- Techniques to drive the simulation
 - by compiled code
 - by events (event-driven)


Performed by the designer,
using the specifications of the
product
Use metrics: **code coverage**
and **node toggling**

Characteristics of a Logic Simulator


- Main features of a logic simulator
 - Accuracy of the results
 - Performance
 - Universality of the models
- Typical cost of a commercial simulator > 50 000€
- Requirements of a logic simulator
 - Logic values
 - Models of the logic elements
 - Technique to drive the simulation

Logic Values


2 logic values:
0 and 1

 

3 logic values:
0, 1 and U

 

5 logic values:
0, 1, U, up and down

 

7

Unknown Logic Value

The initial state of the memory elements is unknown

U = Unknown logic value $\Leftrightarrow \{0,1\}$

Boolean Operations

AND

AND (0, U) =
AND ({0}, {0,1}) =
{AND (0,0), AND (0,1)} =
{0,0} =
0

OR

OR (0, U) =
OR ({0}, {0,1}) =
{OR (0,0), OR (0,1)} =
{0,1} =
U

NOT

NOT (U) =
NOT ({0,1}) =
{NOT (0), NOT (1)} =
{1,0} =
U

8

Three-Valued Algebra

Boolean operations using three logic values

AND	0	1	U
0	0	0	0
1	0	1	U
U	0	U	U

NOT	0	1	U
OUT	1	0	U

OR	0	1	U
0	0	1	U
1	1	1	1
U	U	1	U

Primitive Cubes in Three-Valued Logic

Difference between X and U:

X = don't care

U = unknown

x_1	x_2	x_3	Z
X	1	0	0
1	1	X	0
X	0	X	1
0	1	1	1

Primitive Cubes in Three-Valued Logic

Given the values v_1, v_2, v_3 , where $v_i \in \{0,1,U\}$, determine $Z(v_1, v_2, v_3)$

- Create the cube $v_1 v_2 v_3 \mid X$
- Intersect that cube with the primitive cubes of Z
- If the intersection is consistent, then the value of Z is in the rightmost position
- If the intersection is not consistent, then assign $Z = U$

Examples:

$1U0 \mid X$ not consistent with any cube $\Rightarrow Z = U$


$10U \mid X$ consistent with $X0X \mid 1 \Rightarrow Z = 1$

Intersection operator


\cap	0	1	X	U
0	0	\emptyset	0	\emptyset
1	\emptyset	1	1	\emptyset
X	0	1	X	U
U	\emptyset	\emptyset	U	U

Three-Valued Logic \Rightarrow Lost of Information

 If $B = U$, then $\bar{B} = U$ (B e \bar{B} are not complementary)




 $\Rightarrow F = U$ pessimistic result (correct is $F = 1$)



Shall we use the \bar{U} value? such that: $U \cdot \bar{U} = 0$ and $U + \bar{U} = 1$

Problems with the Unknown Value

 

Incorrect result because U and \bar{U} from different FFs are not complementary


⇒ Better to be pessimistic than incorrect!

Correct solution:

use U_1, U_2, \dots and propagate expressions ⇒ complexity

13

Unknown Value in Functional Models

 

If the control values have **K** unknowns, then it is necessary to perform **2^K** operations on the individual results

(*) Outputs for these addresses are irrelevant


Addresses	Outputs
0000	(*)
0001	(*)
0010	(*)
0011	(*)
0100	(*)
0101	(*)
0110	(*)
0111	(*)
1000	1100
1001	(*)
1010	0100
1011	(*)
1100	0110
1101	(*)
1110	1110
1111	(*)

1UUU → **U1U0**


14

Modeling of Logic Elements

Front-end delay model

 

Back-end delay model

 


Typically $M > N$

15

Delay Model

Inertial and transport delay models

 

Transport delay model: represents a pure propagation delay


Inertial delay model: represents the time for which an input value must be stable before the value is allowed to propagate to the output – filters out unwanted spikes and transients – **default mode in Verilog and VHDL**

16

Delay Models


Min-Max delay model

 e.g. in Verilog: `buf #(3:5:6) (out, in);`
(min:typ:max)




Rise-fall delay model

 e.g. in Verilog: `buf #(2,3) (out, in);`
(rise,fall)



Accurate delay model

 e.g. in Verilog: `buf #(2:3:5,3:4:6) (out, in);`




All these delay models are available in Verilog

17

Models for a Functional Module

 - **Goal:** obtain the result of a logical operation
- Implementation of the model using:
 - Table
 - Algebraic expression
 - Binary decision diagram
 - Procedure



18

Functional Module

Model defined by tables

AND	0	1	U
0	0	0	0
1	0	1	U
U	0	U	U


NOT	0	1	U
OUT	1	0	U

OR	0	1	U
0	0	1	U
1	1	1	1
U	U	1	U

Operations using a three-valued algebra

Functional Module

Model defined by a procedure

 

```
always @(posedge CLK)
begin
  if (RST)
    Q <= 0;
  else if (EN)
    Q <= D;
end
```

Techniques to Drive the Simulation


- by compiled code
Convert the description of the circuit in machine code of the computer (i.e. an executable program)
- by events (event-driven)
Convert the description of the circuit in a set of tables

Modern simulators use a mix of both techniques

Compiled Code Simulation: Overview

- Pre-processing steps
 - Translate the circuit to the canonical form
 - Sort the logic elements \Leftrightarrow levelize the circuit
 - Generate the code for compilation (typically C code)
 - Compile the code to create the simulator
- Levelize the circuit
 - Level 0 is composed by all primary inputs and by the feedback lines that were previously broken
 - Level K is composed by the elements whose inputs are lines with maximum level (K-1)

Levelize the Circuit

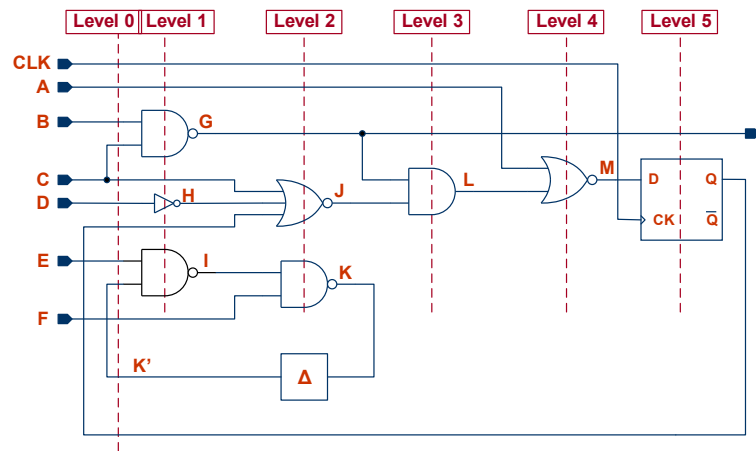

23

Generate the Code for Compilation

```
main ();
{
    K' = <initial value>;
    Q = <initial value>;
    do {
        status = read_inputs (CLK, A, B, C, D, E, F);
        if (status == <no more data>) exit();
        do {
            G = ~(B & C);           /* level 1 */
            H = ~D;                 /* level 1 */
            I = ~(E & K');          /* level 1 */
            J = ~(C | H | Q);       /* level 2 */
            K = ~(I & F);           /* level 2 */
            L = G & J;              /* level 3 */
            M = ~(A | L);           /* level 4 */
            if (CLK) Q = M          /* level 5 */
            if (K' == K)            /* asynchronous signal */
                stable = TRUE;
            else
                stable = FALSE;
            K' = K;
        } while (not stable);
        write_results ();
    } while (true);
}
```


24

Event-Driven Simulation: Overview

- Models of the primitives: gate level or functional level
- Driven by events
- Path selection
- Disadvantages
 - Requires a more complex data structure – dynamic structure
- Advantages
 - Only simulates the elements potentially active (path selection)
 - Allows the simulation of combinatorial and sequential circuits
 - Allows accurate delay processing


25

Event-Driven Simulation: List of Events

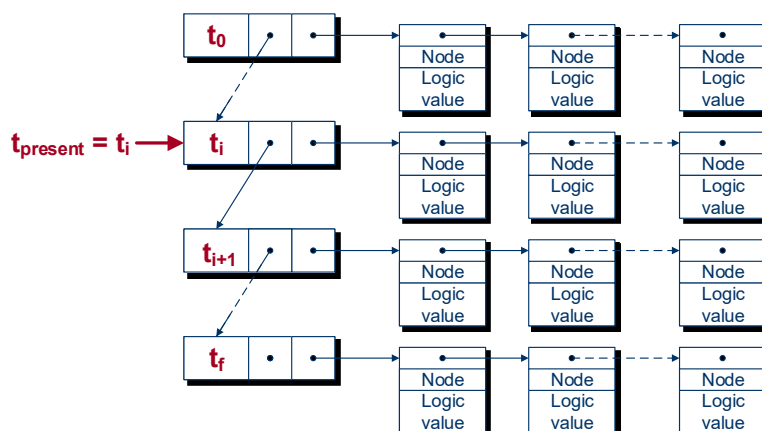


26

Event-Driven Simulation: Algorithm

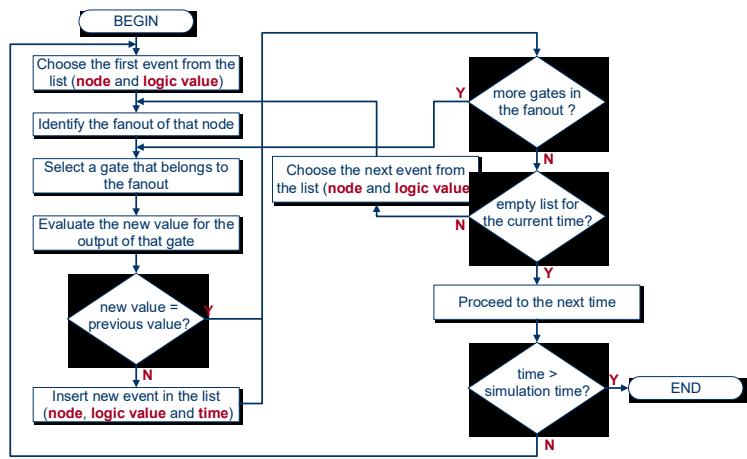

27

Event-Driven Simulation: Buses

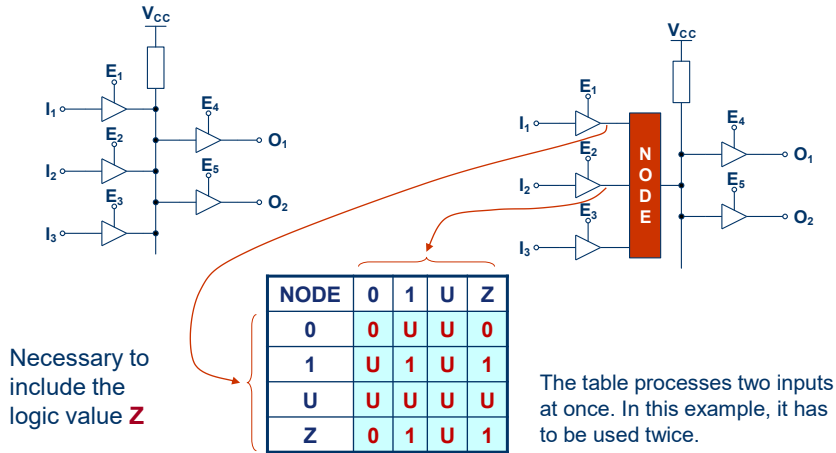

28