

5. FAULT MODELING

Fernando Gonçalves[®]



Projecto, Teste e Fiabilidade de Sistemas Electrónicos – 2019/2020

1

Outline

- Defects
- Realistic faults
- *Stuck-at* fault model
- Fault detection
 - Path sensitization
 - Fault interaction
 - Undetectable faults
 - Redundancy
- Fault equivalence
- Fault collapsing
- Fault dominance



Fernando Gonçalves


Projecto, Teste e Fiabilidade de Sistemas Electrónicos – 2019/2020

2

2

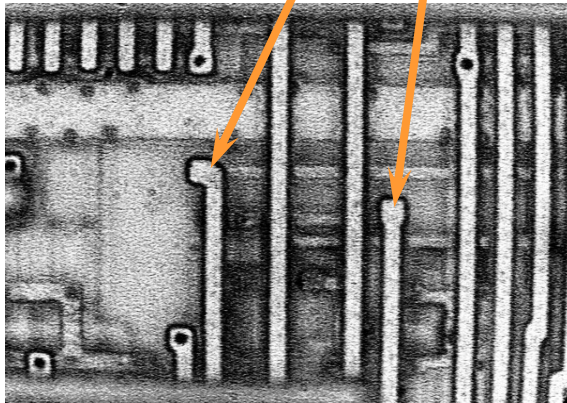
Examples of Manufacturing Defects

Defective contacts \Rightarrow
faults of type "open circuit"




3

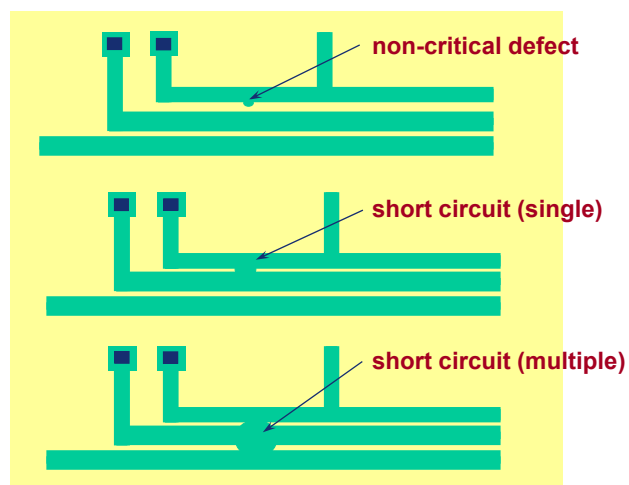Critical Defects vs. Non-Critical Defects



4

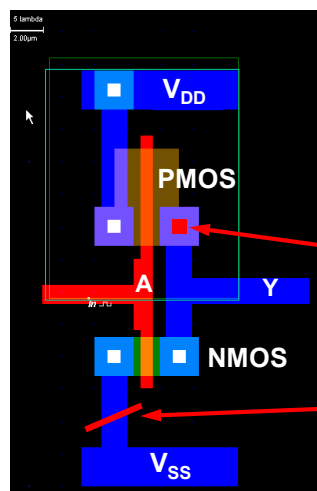Examples of Realistic Faults: Open Circuits




Open contact between metal and diffusion
 $\approx Y\ s-a-0$

Broken metal line
 $\approx Y\ s-a-1$

5

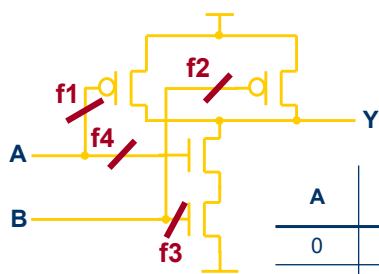Examples of Realistic Faults: Open Circuits




A	B	Y			
		without faults	with f1	with f2	with f3 or f4
0	0	1	1	1	1
0	1	1	previous state	1	1
1	0	1	1	previous state	1
1	1	0	0	0	previous state

In the presence of a fault, a **combinational circuit** can be transformed in a **sequential circuit**

6


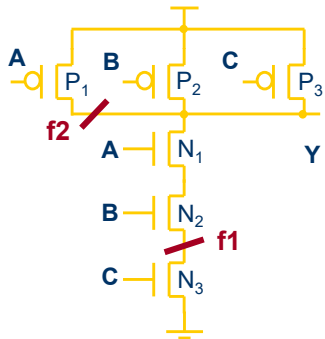
Examples of Realistic Faults: Open Circuits



- Q1: Determine a test vector that makes the fault **f1** observable in Y.
- Q2: How many test vectors detect **f1**?
- Q3: How many test vectors are needed to detect **f2**? Determine the sequence of test vectors.


7

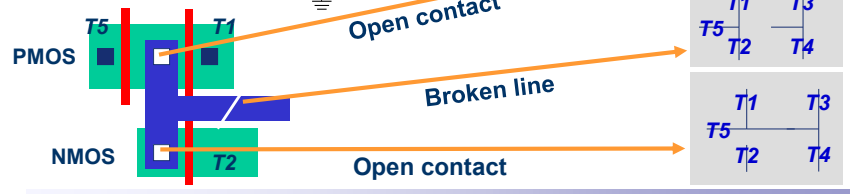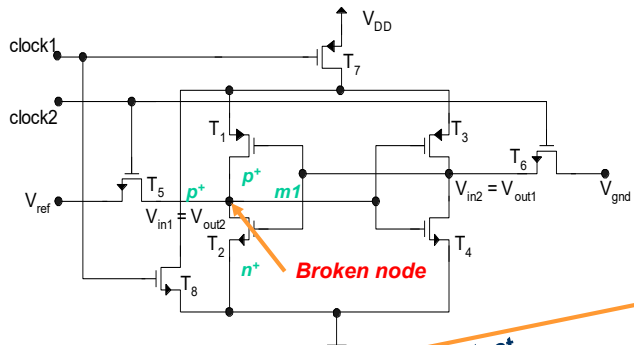Examples of Realistic Faults: Open Circuits



8

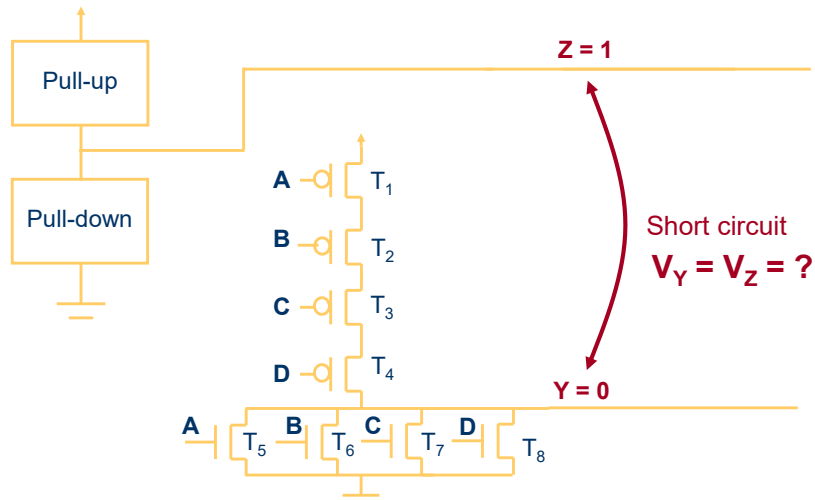Examples of Realistic Faults: *Short Circuits*



The **Single Stuck-At** Fault Model (SSF)


- Is technology independent
- The tests that detect SSFs also detect many physical defects
- The number of SSFs in a circuit is relatively small

Which SSFs to test?

Theorem: In a fanout free circuit, the detection of all SSFs in the primary inputs \Rightarrow detection of all SSFs

Checkpoints: Primary inputs and *fanout* branches

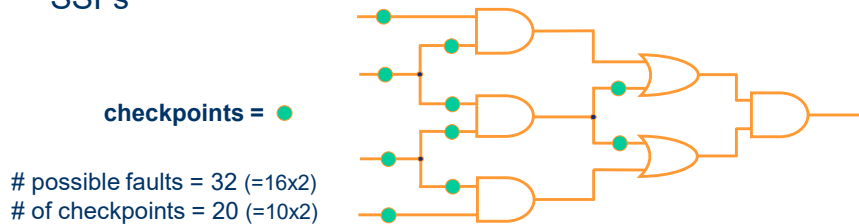Theorem: A set of test vectors that detects all SSFs in all checkpoints of a combinational circuit \Rightarrow detection of all SSFs



11

The Multiple Stuck-At Fault Model (MSF)

How many faults?

assuming n = nbr. of possible fault locations

$\Rightarrow 2n$ SSFs

$\Rightarrow 3^n - 1$ MSFs (any multiplicity)

The multiplicity until k is given by: $\sum_{i=1}^k \binom{n}{i} 2^i$

Example:

$n = 1.000$, $k = 2 \Rightarrow$ approximately 2.000.000 double faults

12

Should we Consider the MSF Model?

- The probability that a physical defect produces a MSF is low
- Experimental results for one circuit shown that a complete set of tests for SSFs also detects more than 99.9% of double, triple and quadruple faults


⇒ so, in general MSFs are not used !

Fault Detection

If a test **t** detects a fault **f**, then $Z(t) \neq Z_f(t)$


For a circuit with a single output, the set of tests that detect the fault **f** are the solutions of the following equation:

$$Z(x) \oplus Z_f(x) = 1$$

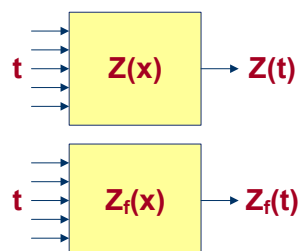

Fault Detection

	Without faults	With fault f
Z_1	$x_1 x_2$	$x_1 + x_2$
Z_2	$x_2 x_3$	$(x_1 + x_2) x_3$

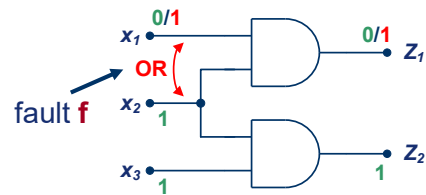

All tests that detect **f** in Z_1

$$x_1 x_2 \oplus (x_1 + x_2) = 1 \Rightarrow x_1 \oplus x_2 = 1$$

All tests that detect **f** in Z_2

$$x_2 x_3 \oplus (x_1 + x_2) x_3 = 1 \Rightarrow x_1 \bar{x}_2 x_3 = 1$$

Line Sensitization

- A line is sensitive to a fault when the logical value is different in the presence of the fault
- A sensitive line highlights the effect of a fault
- The values in the fault-free and faulty circuits are denoted according to the following notation:


<value for fault-free circuit> / <value for faulty circuit>

Example: **0/1** \Rightarrow '0' in the fault-free circuit

'1' in the faulty circuit

Path Sensitization

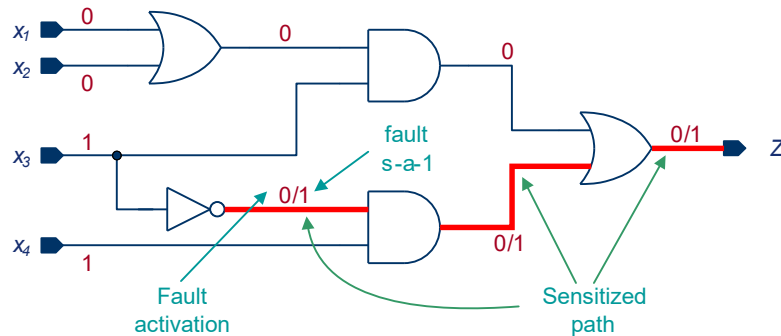
A sensitized path has different logical values in the presence of a fault



17

Fault Detection

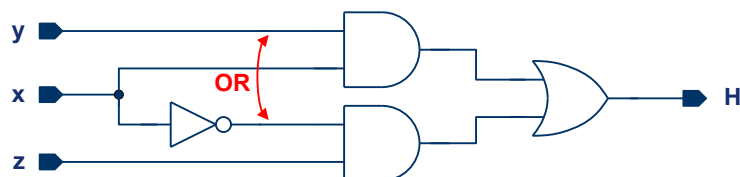If **f is detectable**, then there is at least a test that detects **f**
Otherwise, **f is undetectable** $\Leftrightarrow H = H_f$



$$H = x y + \bar{x} z$$

$$H_f = x (\bar{x} + y) + (\bar{x} + y) z = x y + \bar{x} z + y z = x y + \bar{x} z$$


$$H = H_f \Rightarrow \mathbf{f \text{ is undetectable}}$$

Are there any problems with undetectable faults?


18

Fault Interaction

The test $xyz = 111$ detects **q s-a-0**

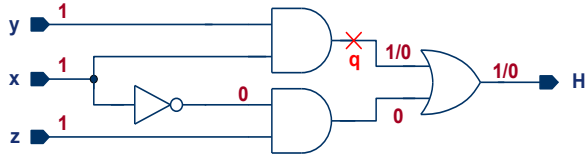

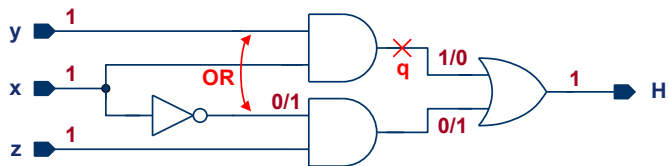
But $xyz = 111$ does not detect **q s-a-0** in the presence of another undetectable fault \Rightarrow **fault masking** might exist, even when one of the faults is undetectable



Redundancy and Detection

$$H = x y + \bar{x} z + y z = x y + \bar{x} z$$
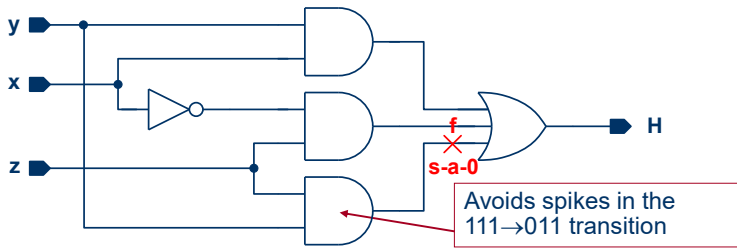
$$H_f = x y + \bar{x} z \Rightarrow f \text{ is undetectable}$$



All combinational circuits with undetectable stuck-at faults can be simplified

In an irredundant circuit, all stuck-at fault are detectable

Disadvantages of Redundancy


- Testability ↓
- Complexity of Automatic Test Pattern Generation (ATPG) ↑↑
- Fault coverage evaluation ↑
- Circuit area ↑
- Propagation delays ↑
- Power consumption ↑
- Manufacturing yield ↓

Is redundancy always disadvantageous?

21

Triple Redundancy

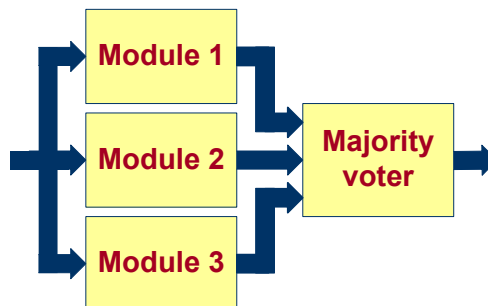Modules 1, 2 e 3 have identical functionalities, but the implementations are distinct




The triple redundancy ...

- is widely used in the design of critical systems
- has a negative impact in the system cost (larger silicon area or larger number of components)
- is an alternative to the on-line testing

22

Fault Equivalence

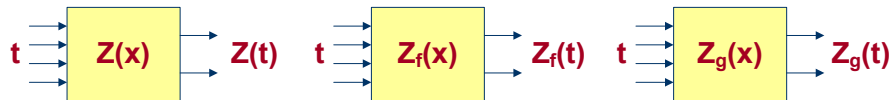

f and **g** are functionally equivalent if: $(f \equiv g) \Leftrightarrow Z_f(x) = Z_g(x)$

t distinguishes between **f** and **g** $\Leftrightarrow Z_f(t) \neq Z_g(t)$

For a circuit with a single output, the **set of all tests that distinguish between f and g** are the solutions of:

$$Z_f(x) \oplus Z_g(x) = 1$$


23

Examples of Fault Equivalence

f: Short circuit between A and B (wired-and)

g: Z s-a-0


$\Rightarrow f \equiv g$

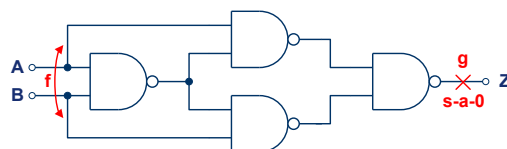

f: A s-a-1


g: B s-a-1

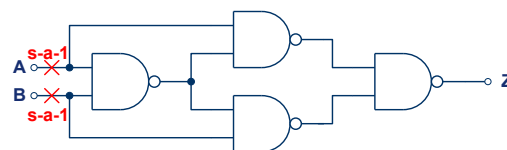\Rightarrow set of tests that distinguish between f and g: $\bar{A} \oplus \bar{B} = 1$




24

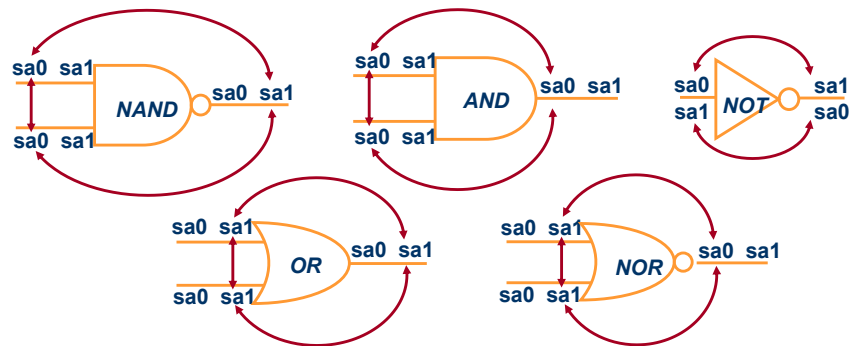Fault Collapsing based on Fault Equivalence



Fault Collapsing: A **representative fault** is selected from each set of equivalent faults. The remaining faults can be deleted. The weight of the **representative fault** must be equivalent to the weights of the collapsed faults.

Example of Fault Collapsing

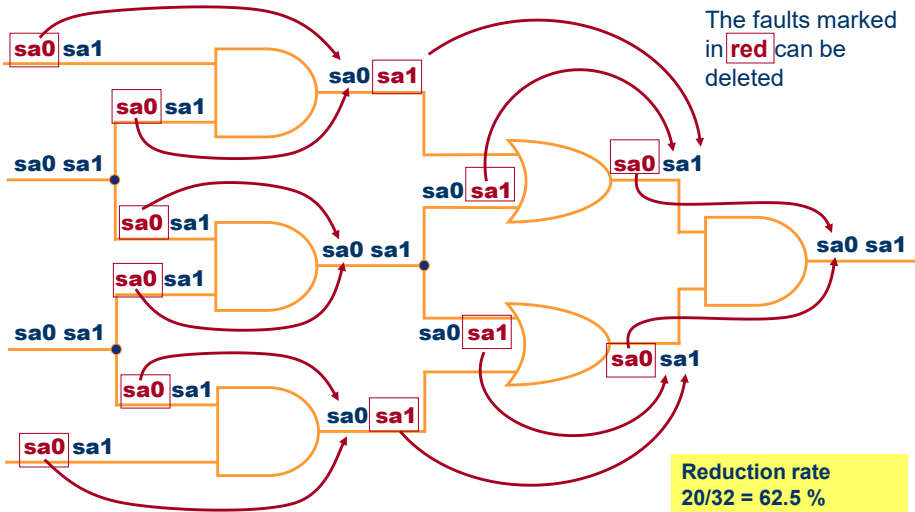


Fault Dominance

- If all tests that detect **f1** also detect **f2**, then we can state that **f2 dominates f1**
- If a fault **f2 dominates f1**, then **f2 can be deleted** from the fault list
- If two faults dominate mutually, then those faults are equivalent


$$T_{f1} = \{\text{all tests that detect } f1\}$$
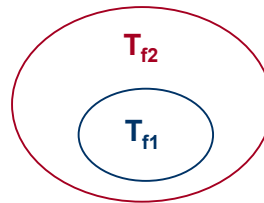
$$T_{f2} = \{\text{all tests that detect } f2\}$$





27

Example of Fault Dominance

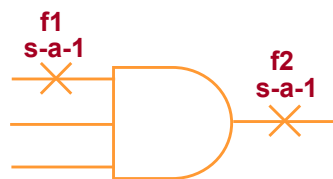

f2 dominates f1
f2 can be deleted

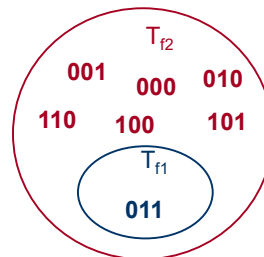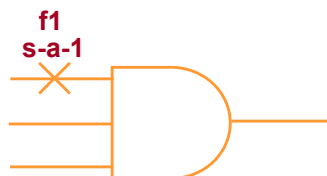

The fault dominance rules can be also used to perform fault collapsing

28

Fault Collapsing and Dominance: Summary



○ s-a-0 ● s-a-1

n inputs $\Rightarrow 2(n + 1)$ faults (single stuck-at)

but $n + 1$ faults can be deleted by fault equivalence or fault dominance

